Digital Clock Implementation using Arduino with Multiplexing and Editing Features

Dhawal

Department of Electrical Engineering Indian Institute of Technology Hyderabad Email: ee24btech11015@iith.ac.in

Electrical Engineering Department Indian Institute of Technology, Hyderabad



Outline

- Introduction
- Components
- Circuit Connections
- Multiplexing Technique
- Digit Editing Logic
- 6 Increment Logic and Truth Tables
- Decrement Logic
- 8 Hardware Build
- Onclusion

Introduction

- Digital clock system with editing features using Arduino
- Multiplexing six 7-segment displays using minimal I/O pins
- Pause/play functionality and digit-by-digit editing
- Boolean logic for increment/decrement and constraints for each digit

Components List

Component	Value	Quantity
Arduino Uno		1
USB Cable	Type B	1
Seven Segment Display	Common Cathode	6
Push Buttons		4
IC 7447		1
Jumper Wires	M-M	16
Breadboard		1
Resistors	220Ω	7
Resistors	$10k\Omega$	4



Arduino Pin Connections

ltem	Arduino Pin	Function
Button 1	D10	Edit Mode Toggle
Button 2	D11	Next Digit Selection
Button 3	D12	Increment Digit
Button 4	D13	Decrement Digit
IC 7447 Pin 7	D0	BCD Bit 0 (A)
IC 7447 Pin 1	D1	BCD Bit 1 (B)
IC 7447 Pin 2	D2	BCD Bit 2 (C)
IC 7447 Pin 6	D3	BCD Bit 3 (D)
Display 1	D4	Hours Tens Digit
Display 2	D5	Hours Units Digit
Display 3	D6	Minutes Tens Digit
Display 4	D7	Minutes Units Digit
Display 5	D8	Seconds Tens Digit
Display 6	D9	Seconds Units Digit

Multiplexing

- All BCD inputs shared among six 7-segment displays
- Arduino controls enable pins D4-D9
- ullet Each digit displayed for 1ms o appears continuous
- Saves I/O pins, enables six-digit display

Editing System


- PAUSE button toggles run/edit mode
- NEXT button selects which digit to edit
- 3 INC button increments selected digit (rollover constraints)
- DEC button decrements selected digit (rollunder constraints)
- Selected digit blinks every 500ms

Digit Constraints

- Seconds/Minutes Ones: 0–9
- Seconds/Minutes Tens: 0–5
- Hours Ones: 0-9 (if tens = 0/1), 0-3 (if tens = 2)
- Hours Tens: 0–2

Seconds / Minutes / Hours (Tens= 0/1) Ones (0-9)


Z	Υ	Χ	W	D	С	В	Α
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

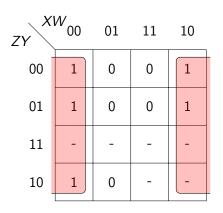

ZY	W ₀₀	01	11	10
00	0	1	0	1
01	0	1	0	1
11	-	-	-	-
10	0	0	-	-

$$A = W_1'$$

$$B = (W_1 X_1' Z_1') + (W_1' X_1)$$

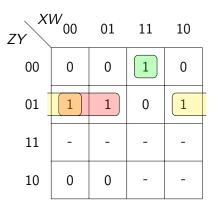


ZY	W ₀₀	01	11	10
00	0	0	0	0
01	0	0	1	0
11	-	-	_	-
10	1	0	-	-

$$C = (X_1'Y_1) + (W_1'Y_1) + (W_1X_1Y_1')$$

$$D = (W_1'Z_1) + (W_1X_1Y_1)$$

Seconds / Minutes Tens (0-5)


Z	Υ	Χ	W	D	С	В	Α
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	0	0	0

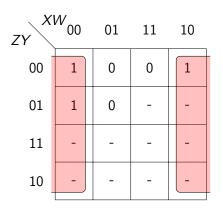

ZY	N ₀₀	01	11	10
00	0	1	0	1
01	0	0	-	-
11	-	-	-	-
10	-	-	-	-

$$A = W_2'$$

$$B = (W_2 X_2' Y_2') + (W_2' X_2)$$

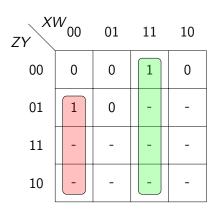


$$D = 0$$


$$C = (W_2X_2) + (W_2'X_2'Y_2)$$



Hours Ones (Tens = $2 \rightarrow 0-3$)

Χ	W	D	С	В	Α
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
1	1	0	0	0	0

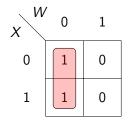


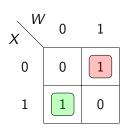


$$A = W'_5$$
 $B = (W_5 X'_5) + (W'_5 X_5)$ $C = 0$ $D = 0$ (1)

Hours Tens (0-2)

Χ	W	D	С	В	Α
0	0	0	0	0	1
0	1	0	0	0	0
1	0	0	0	0	0

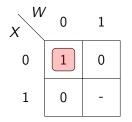

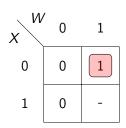


$$A = W_6' X_6'$$

$$C = 0$$

$$D = 0$$
(2)


Seconds / Minutes / Hours (Tens= 0/1) Ones (0-9)


Z	Υ	Χ	W	D	С	В	Α
0	0	0	0	1	0	0	1
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	1
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	1
0	1	1	1	0	1	1	0
1	0	0	0	0	1	1	1
1	0	0	1	1	0	0	0

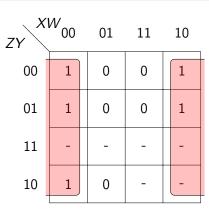

$$A = W_1'$$
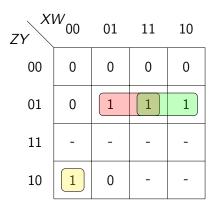
$$B = (X_1'W_1'((Z_1'Y_1) + (Z_1Y_1'))) + (Z_1'W_1X_1') + (Z_1$$




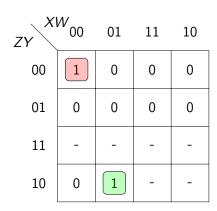


$$C = (Z_1'Y_1(X_1 + W_1)) + (Z_1X_1'W_1'Y_1') \qquad D = X_1'Y_1'((Z_1W_1) + (Z_1'W_1'))$$

Seconds / Minutes Tens (0-5)


Z	Υ	Χ	W	D	С	В	Α
0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	1
0	1	0	1	0	1	0	0

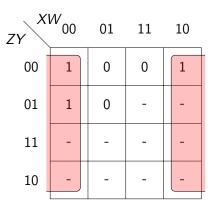

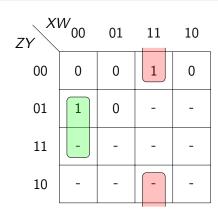

$$A = W_2'$$

$$B = (Y_2 X_2' W_2') + (Y_2' X_2 W_2)$$

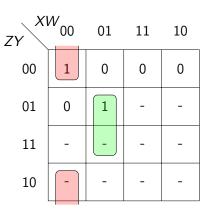


$$D = 0$$


$$C = X_2'((Y_2W_2) + (Y_2'W_2'))$$



Hours Ones (Tens = $2 \rightarrow 0-3$)

Χ	W	D	С	В	Α
0	0	0	0	1	1
0	1	0	0	0	0
1	0	0	0	0	1
1	1	0	0	1	0

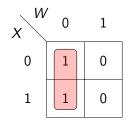


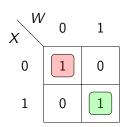


$$A = W'_5$$
 $B = (X_5 W_5) + (X'_5 W'_5)$ $C = 0$ $D = 0$ (3)

Hours Tens (0-2)

Χ	W	D	С	В	Α
0	0	0	0	1	0
0	1	0	0	0	0
1	0	0	0	0	1

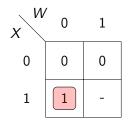

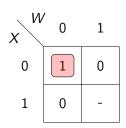

$$A = X_6 W_6'$$

$$C = 0$$

$$D = 0$$
(4)

Hardware Implementation

- Connect seven-segment displays to breadboard
- Connect all segment outputs together (through resistors)
- Make connections to IC7447 and buttons to Arduino
- Add current-limiting resistors for LEDs
- Add pull-down resistors for buttons


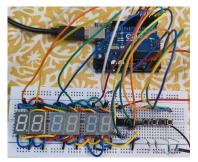


Figure: Final Arduino-based Clock Implementation

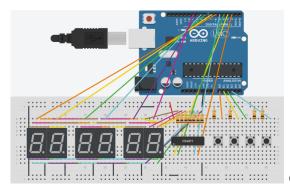

Tinkercad Simulation



Clock Tinkercad Simulation

Summary

- Successfully implemented digital clock with editing features
- Efficient multiplexing and minimal I/O usage
- Complete increment/decrement logic implemented via Boolean expressions
- Full digit-by-digit editing with constraints for hours, minutes, seconds

Acknowledgment

The complete source code and documentation can be found at: https://github.com/Dhawal24112006/projects.git

Thank You!

