

Digital Clock using the Arduino Framework

Dhawal Saini and G. V. V. Sharma
 Department of Electrical Engineering
 Indian Institute of Technology Hyderabad
 Email: gadepall@ee.iith.ac.in

Abstract—In this paper the design and implementation of a feature-rich digital clock is demonstrated. The system uses multiplexing to drive six seven-segment displays efficiently, minimizing I/O utilization. Key functionalities include timekeeping, digit-by-digit editing, and pause/play control. Boolean-based increment and decrement logic ensures more accurate cascading of seconds, minutes, and hours within standard constraints. The hardware setup, complemented by software debouncing and display refreshing, demonstrates a reliable, compact, and user-interactive digital clock suitable for both educational and practical applications.

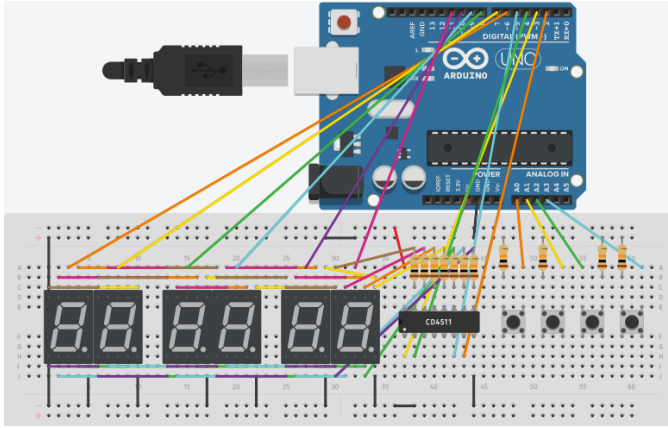


Fig. 1: Tinkercad Simulation of the Digital Clock

I. INTRODUCTION

Digital timekeeping has long been a critical component of electronic system design, with classical digital design principles thoroughly discussed in foundational works such as [1]–[3]. The advent of microcontroller platforms, particularly Arduino, has enabled the development of compact, programmable clocks with enhanced user interactivity [4]. Techniques such as BCD-to-seven-segment interfacing and display multiplexing allow efficient utilization of limited I/O resources while maintaining accurate visual representation [5]. Inspired by these principles, a simple state machine representing a decade counter is implemented in [6]. Based on this, we design an Arduino-based digital clock featuring six-digit multiplexed displays, pause/play functionality, and digit-by-digit editing with Boolean logic-driven increment and decrement operations.

II. CLOCK FUNCTIONALITY AND HARDWARE SETUP

Fig. 1 shows the various hardware connections and the corresponding components are listed in Table II. The clock

follows the 23:59:59 format using 6 displays. The first 2 represent hours, next 2 denote minutes and the last 2 count the seconds. The six displays are connected to the arduino through the pin connections listed in Table I. The number count for each display is also listed therein. Pin connections from the

| Display | Arduino Pin | Description |
|---------|-------------|---|
| 1 | D4 | Counts 0-2 |
| 2 | D5 | Counts $\begin{cases} 0-3 & \text{display1} = 2, \\ 0-9 & \text{otherwise} \end{cases}$ |
| 3 | D6 | Counts 0-5 |
| 4 | D7 | Counts 0-9 |
| 5 | D8 | Counts 0-5 |
| 6 | D9 | Counts 0-9 |

TABLE I: Display to Arduino Connections

Arduino to the four push buttons are available in Table III. Table IV gives the connections between the Arduino and the IC 7447 display decoder. Further, the pin connections for the IC 7447 to all the displays are available in Table V.

| Component | Value | Quantity |
|-----------------------|--------------------------|----------|
| Arduino Uno | | 1 |
| USB Cable | Type B | 1 |
| Seven Segment Display | Common Cathode | 6 |
| Push Buttons | | 4 |
| IC 7447 | | 1 |
| Jumper Wires | M-M | 16 |
| Breadboard | | 1 |
| Resistors | 220 Ω | 7 |
| Resistors | 10k Ω (pull-down) | 4 |

TABLE II: Components List

| Button | Arduino Pin | Description |
|--------|-------------|----------------------|
| 1 | D10 | Edit Mode Toggle |
| 2 | D11 | Next Digit Selection |
| 3 | D12 | Increment Digit |
| 4 | D13 | Decrement Digit |

TABLE III: Button to Arduino Connections

| IC 7447 PIN | Arduino Pin | Description |
|-------------|-------------|---------------|
| 7 | D0 | BCD Bit 0 (A) |
| 1 | D1 | BCD Bit 1 (B) |
| 2 | D2 | BCD Bit 2 (C) |
| 6 | D3 | BCD Bit 3 (D) |

TABLE IV: IC 7447 to Arduino Connections

| Z | Y | X | W | D | C | B | A |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |

| ZY | XW | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 1 | 0 | 0 | 1 |
| 01 | 1 | 0 | 0 | 1 |
| 11 | - | - | - | - |
| 10 | 1 | 0 | - | - |

(a) $A = W'_1$

| ZY | XW | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 1 | 0 | 1 |
| 01 | 0 | 1 | 0 | 1 |
| 11 | - | - | - | - |
| 10 | 0 | 0 | - | - |

(b) $B = W_1 X'_1 Z'_1 + W'_1 X_1$

| ZY | XW | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 1 | 0 |
| 01 | 1 | 1 | 0 | 1 |
| 11 | - | - | - | - |
| 10 | 0 | 0 | - | - |

(c) $C = X'_1 Y_1 + W'_1 Y_1 + W_1 X_1 Y'_1$

| ZY | XW | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 1 | 0 |
| 11 | - | - | - | - |
| 10 | 1 | 0 | - | - |

(d) $D = W'_1 Z_1 + W_1 X_1 Y_1$

Fig. 2: Counting 0-9

| IC 7447 | Seven Segment (All) |
|---------|---------------------|
| 13 | a |
| 12 | b |
| 11 | c |
| 10 | d |
| 9 | e |
| 15 | f |
| 14 | g |
| 8 | Ground |
| 16 | 5V |

TABLE V: BCD to 7-Segment Connections

III. CLOCK LOGIC

Here, we discuss how to design counters for the various displays in the clock.

A. Displays 2 ($Display1 \neq 2$), 4 and 6

These displays count from 0-9. Display 2 will do this only when Display 1 is less than 2. The truth table and the corresponding K-maps using dont cares for the output variables are given in Fig. 2 along with the corresponding logic equations.

B. Displays 3 and 5

These displays count from 0-5. The truth table and the corresponding K-maps using dont cares for the output variables are given in Fig. 3, along with the corresponding logic equations. $D = 0$ in this case.

C. Display 2 ($Display1 = 2$)

This display counts from 0-3, when the first display shows 2. The truth table and the corresponding K-maps using dont cares for the output variables are given in Fig. 4. along with the corresponding logic equations. $C = D = 0$ in this case.

D. Display 1

This display counts from 0-2, representing the first digit of the hour. The truth table and the corresponding K-maps using dont cares for the output variables are given in Fig. 5, along with the corresponding logic equations. $C = D = 0$ in this case.

IV. CONTROL LOGIC AND IMPLEMENTATION

A. Decrement Logic

This logic is primarily used to decrease the count on a particular display using button 4. This is helpful in setting the time for the clock. The relevant truth tables and resulting Boolean equations using K-maps following the approach in the previous section are available in Table VI.

B. Multiplexing Technique

All BCD inputs (A-D) are shared among six seven-segment displays. Displays are enabled one at a time using $EN[0..5] = D4-D9$ (see Table I). Each digit is displayed for 1ms, creating a fast alternating effect that appears continuous. This saves I/O pins and allows full six-digit display.

| Z | Y | X | W | D | C | B | A |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |

$$A = W'_1 \quad (1)$$

$$B = (X'_1 W'_1 ((Z'_1 Y_1) + (Z_1 Y'_1))) + (Z'_1 W_1 X_1) \quad (2)$$

$$C = (Z'_1 Y_1 (X_1 + W_1)) + (Z_1 X'_1 W'_1 Y'_1) \quad (3)$$

$$D = X'_1 Y'_1 ((Z_1 W_1) + (Z'_1 W'_1)) \quad (4)$$

| Z | Y | X | W | D | C | B | A |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |

$$A = W'_2 \quad (5)$$

$$B = (Y_2 X'_2 W'_2) + (Y'_2 X_2 W_2) \quad (6)$$

$$C = X'_2 ((Y_2 W_2) + (Y'_2 W'_2)) \quad (7)$$

$$D = 0 \quad (8)$$

| X | W | D | C | B | A |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 |

$$A = W'_5 \quad (9)$$

$$B = (X_5 W_5) + (X'_5 W'_5) \quad (10)$$

$$C = D = 0 \quad (11)$$

| X | W | D | C | B | A |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |

$$A = X_6 W'_6 \quad (12)$$

$$B = X'_6 W'_6 \quad (13)$$

$$C = D = 0 \quad (14)$$

TABLE VI: Truth Tables for decrementing displays

C. Digit Editing

The clock allows pausing and digit-by-digit editing (See Table III).

- 1) Press PAUSE (D10) to toggle run/edit mode. In edit mode, the clock stops.
- 2) Press NEXT (D11) to select the digit to edit (cycles 0-5: sec1, sec10, min1, min10, hr1, hr10).
- 3) Press INC (D12) to increment the selected digit with rollovers.
- 4) Press DEC (D13) to decrement the selected digit with rollunders.
- 5) Selected digit blinks every 500ms to indicate focus.

| Z | Y | X | W | D | C | B | A |
|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |

| ZY | XW | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 1 | 0 | 0 | 1 |
| 01 | 1 | 0 | - | - |
| 11 | - | - | - | - |
| 10 | - | - | - | - |

(a) $A = W'_2$

| ZY | XW | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 1 | 0 | 1 |
| 01 | 0 | 0 | - | - |
| 11 | - | - | - | - |
| 10 | - | - | - | - |

(b) $B = W_2X'_2Y'_2 + W'_2X_2$

| ZY | XW | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 1 | 0 |
| 01 | 1 | 0 | - | - |
| 11 | - | - | - | - |
| 10 | - | - | - | - |

(c) $C = W_2X_2 + W'_2X'_2Y'_2$

Fig. 3: Counting 0-5

| X | W | D | C | B | A |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 |

| X | W | |
|---|---|---|
| | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 1 | 0 |

(a) $A = W'_5$

| X | W | |
|---|---|---|
| | 0 | 1 |
| 0 | 0 | 1 |
| 1 | 1 | 0 |

(b) $B = W_5X'_5 + W'_5X_5$

Fig. 4: Counting 0-3

| X | W | D | C | B | A |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 |

| | | | |
|---|---|---|---|
| | W | 0 | 1 |
| X | | | |
| 0 | | 1 | 0 |
| 1 | | 0 | - |

(a) $A = W'_6 X'_6$

| | | | |
|---|---|---|---|
| | W | 0 | 1 |
| X | | | |
| 0 | | 0 | 1 |
| 1 | | 0 | - |

(b) $B = W_6 X'_6$

Fig. 5: Counting 0–2

D. Implementation

Pressing Button 1 toggles between run mode and edit mode. In edit mode, the clock pauses. Following functions are available in edit mode. The selected digit blinks at 5Hz (200ms on, 200ms off) for visual feedback.

- 1) Pressing Button 2 selects the next digit for editing (cycles through all six digits).
- 2) Pressing Button 3 increments the currently selected digit using the increment logic tables.
- 3) Pressing Button 4 decrements the currently selected digit using the decrement logic tables.

V. SOFTWARE

Following are the steps to upload code to the Arduino

- 1) Connect Arduino to computer via USB
- 2) Upload the following code to the Arduino

<https://github.com/gadepall/clock/blob/main/codes/code.cpp>

The Arduino code implements

- Timer interrupt for clock ticking (10Hz interrupt rate)
- Button debouncing with software delays
- Multiplexed display refresh
- Editing mode with digit selection and value modification using the Boolean logic from the tables
- Proper constraints on time values (hours 0-23, minutes 0-59, seconds 0-59)

VI. FUTURE WORK

The clock prototype on the Arduino is the first step towards building a chip. The next step is to adapt the current design for implementation on a Vaman FPGA with a QuickLogic SoC and use additional EDA tools for physical chip design. This will be done in future work.

REFERENCES

- [1] M. M. Mano, *Digital Design*, 5th ed. Pearson, 2013.
- [2] A. Malvino and D. Leach, *Digital Principles and Applications*, 8th ed. McGraw-Hill, 2017.
- [3] D. A. Patterson and J. L. Hennessy, *Computer Organization and Design*, 5th ed. Morgan Kaufmann, 2014.
- [4] Arduino Documentation, *Arduino Reference*, 2025, accessed: October 21, 2025. [Online]. Available: <https://www.arduino.cc/reference/en/>
- [5] Texas Instruments, *Datasheet for IC 7447*, 2025, accessed: October 21, 2025. [Online]. Available: <https://www.ti.com/product/7447>
- [6] G. V. V. Sharma, *Digital Design through Arduino*, 3rd ed. Narayanpal Prakashan, 2025.